

Triodenbereich: $V_{DS} < V_{GS} - V_{th}$, $I_D = \frac{W}{L} k_n (V_{GS} - V_{th} - \frac{1}{2} V_{DS}) V_{DS}$

Sättigung: $V_{DS} \geq V_{GS} - V_{th}$, $I_D = \frac{W}{L} k_n (V_{GS} - V_{th})^2$



Unterschwell: $V_{GS} \leq V_{th}$, $I_D = \frac{W}{L} k_n 10^{(\frac{V_{GS}-V_{th}}{S})} [1 - \exp(-\frac{V_{DS}}{Lk_n})]$

$$I_{DS} = \frac{W}{L} k_n (V_{GS} - V_{th})$$

bei Transistor:


$$I_{DS} = \frac{W}{L} k_n (V_{GS} - V_{th})$$

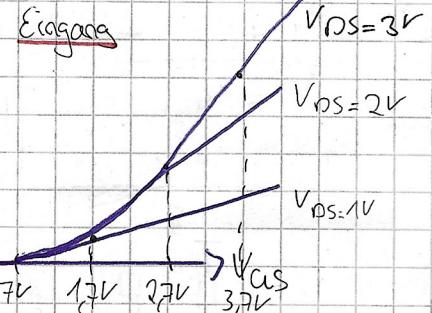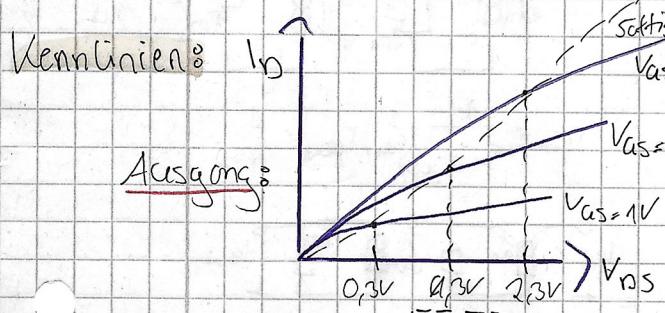p-Mos: $I_{DS} = -k_p \frac{W}{L} V_{DS}$



$$C_0 I = j \omega C U$$

$$I = U / j \omega L$$

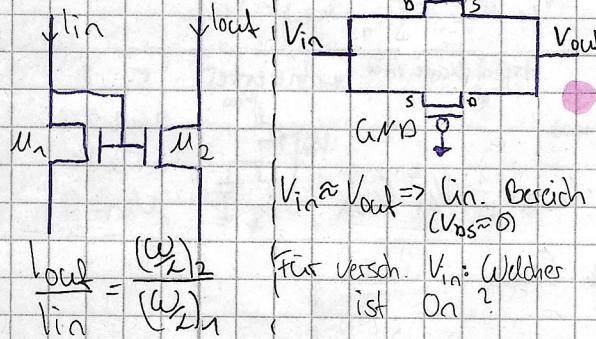

Sourceschaltung: Source auf Masse

$$g_{dsn} = \frac{W}{L} k_n (V_{GS} - V_{th})$$

$$V_{cat} = -g_{m} V_{in} \frac{R_o}{R_o + R_D} \quad \text{für aktiver Betrieb}$$


$$g_{dsp} = \frac{W}{L} k_p (1 - V_{GS} - V_{th})$$

$$(\approx -g_m V_{in} R_D \quad (R_o \gg R_D)) \quad \text{für Sättigung}$$




$$r_{ein} = R_G \approx \infty$$

$$g_m = \frac{W}{L} k_n (V_{GS} - V_{th})$$


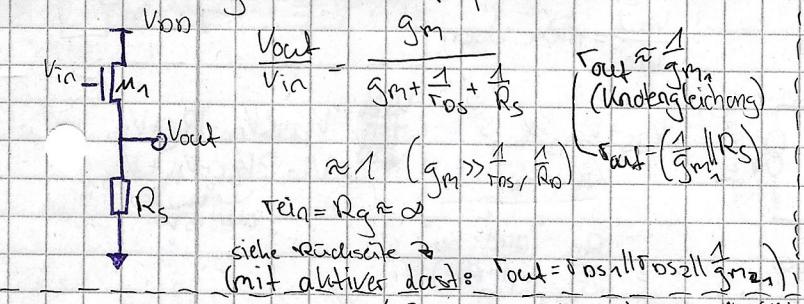
Drainschaltung: Drain auf festem Potential



Gateschaltung: Gate auf festem Potential

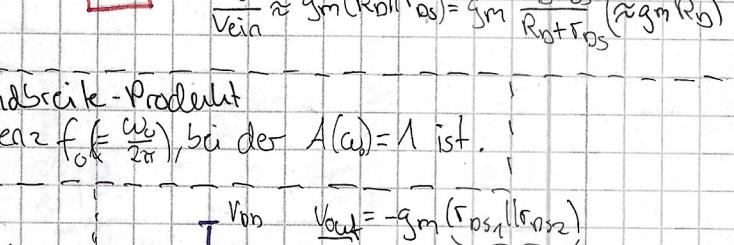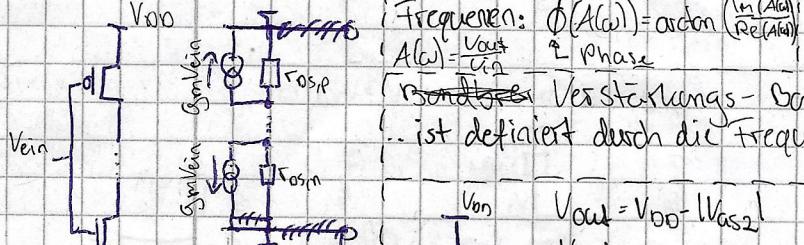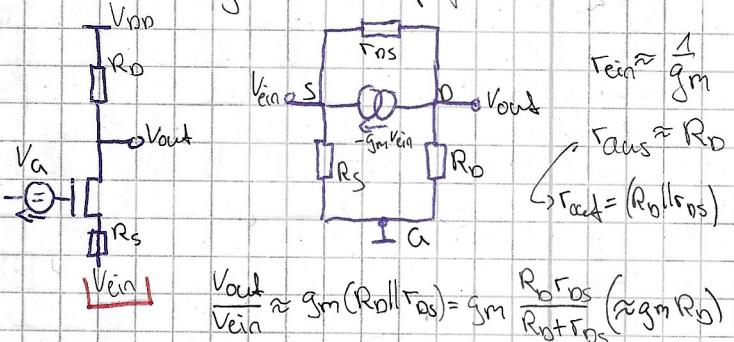


Source-Folger

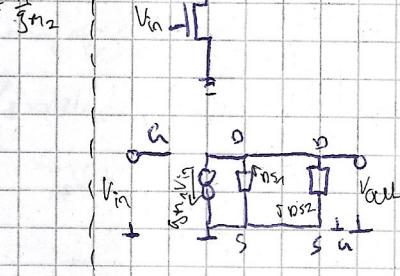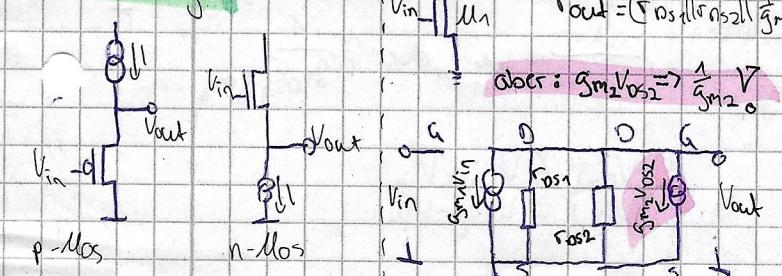

$$\begin{aligned}
 V_{out} &= g_{m1}(V_{in} - V_{out})(\frac{1}{R_{DS1}} + \frac{1}{R_{DS2}}) \\
 &= \frac{g_{m1}(\frac{1}{R_{DS1}} + \frac{1}{R_{DS2}})}{1 + g_{m1}(\frac{1}{R_{DS1}} + \frac{1}{R_{DS2}})} \approx 1 \\
 R_{out} &= \frac{V_x}{I_x} = \frac{\frac{1}{R_{DS1}} + \frac{1}{R_{DS2}}}{1 + g_{m1}(\frac{1}{R_{DS1}} + \frac{1}{R_{DS2}})} \approx \frac{1}{g_{m1}}
 \end{aligned}$$



$$\begin{aligned}
 V_{out} &= V_{DD} - I_D \cdot R_D \\
 &= V_{DD} - g_{m1} \cdot V_{in} \cdot R_D \\
 &= V_{DD} - g_{m1} \cdot V_{in} \cdot (\frac{1}{R_{DS1}} + \frac{1}{R_{DS2}}) \\
 R_{out} &= \frac{V_x}{I_x} = \frac{\frac{1}{R_{DS1}} + \frac{1}{R_{DS2}}}{1 + g_{m1}(\frac{1}{R_{DS1}} + \frac{1}{R_{DS2}})} \approx \frac{1}{g_{m1}}
 \end{aligned}$$

Differenzstufen: Diff-Verstärker

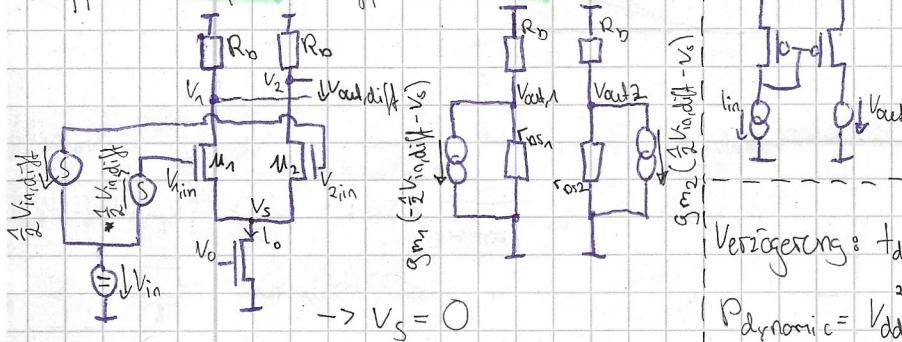

$$V_{out,diff} = V_{2,out} - V_{1,out} \Rightarrow \frac{V_{out,diff}}{V_{i_0,diff}} = -g_m(R_D1 || R_D2)$$



Gleichaktverstärker

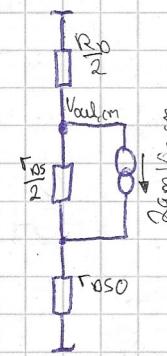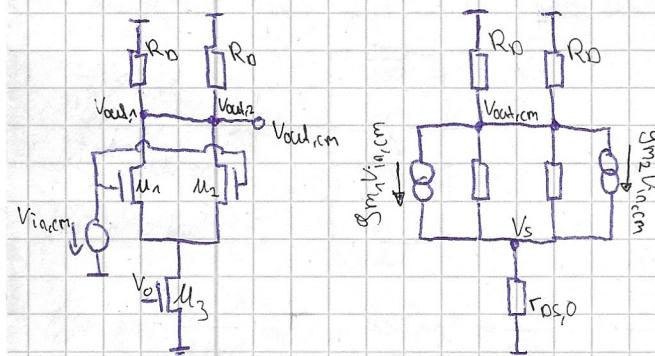

$$\frac{V_{out}}{V_{in}} = \text{siehe oben}$$

$$V_{OS} = V_{in,2} - V_{in,1} = V_{th,1} - V_{th,2}$$
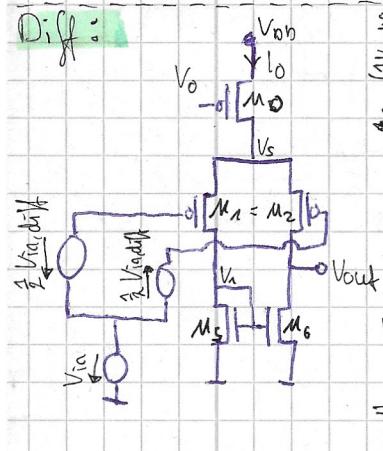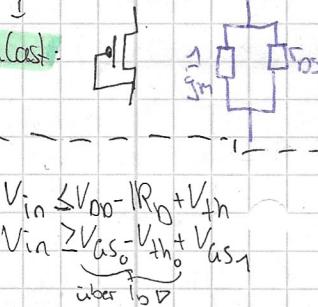
$$= \frac{R_D}{2 \cdot R_{DS3}} \quad (\text{auch bei P-Mos})$$




$$\begin{aligned}
 V_{out} &= -\left(\frac{1}{2} g_{m2} V_{i_0,diff} + g_{m1} V_1\right) \left(\frac{1}{R_{DS2}} + \frac{1}{R_{DS3}}\right) \\
 &= -g_{m2} V_{i_0,diff} \left(\frac{1}{R_{DS2}} + \frac{1}{R_{DS3}}\right)
 \end{aligned}$$

$$\text{Für Sättigung: } V_{in} \leq V_{DD} - |V_{AS}| + |V_{AS}| + V_{th}$$

$$V_{in} \geq V_{AS} - V_{th}$$
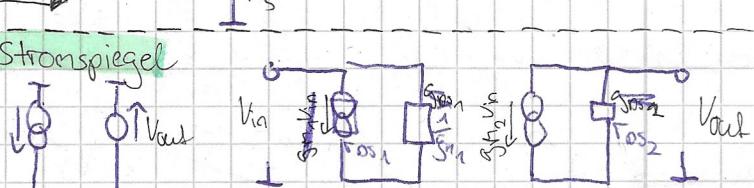
$$\begin{aligned}
 \frac{V_{out}}{V_{in}} &= -\frac{g_m R_D}{R_{DS1} + R_{DS2} + R_S + g_m R_D} \\
 &\approx \frac{g_m R_D}{1 + g_m R_S} \\
 R_{out} &= R_D \parallel (g_m R_S + R_S + R_D) \approx R_D \quad (R_D \ll \dots)
 \end{aligned}$$



$$R_{in} = \frac{1}{g_{m1} + g_{m2}} \approx \frac{1}{g_{m1}}, \quad R_{out} = \frac{1}{g_{m2}}$$

$$\begin{aligned}
 R_{in} &= \frac{1}{g_{m1} + g_{m2}} \approx \frac{1}{g_{m1}}, \quad R_{out} = \frac{1}{g_{m2}} \\
 \text{treibt Kapazität} & \\
 \text{Inverter} & \\
 R_{in}: & \quad V_{in} \neq 0 \\
 V_{out} \neq 0 & \\
 R_{out}: & \quad V_{in} = 0
 \end{aligned}$$

Verzögerung: $t_d \sim R_{DS} C_{load}$


$$P_{dynamic} = \frac{1}{2} V_{dd}^2 \cdot f_{clock} \cdot C_{load} = \frac{1}{2} V_{dd}^2 \cdot C_{load}$$

$$\frac{E_1}{E_2} < 0 \rightarrow E_1 < E_2$$

$$\frac{V_{out}}{V_{in}} = \text{siehe oben}$$

$$\begin{aligned}
 V_{OS} &= V_{in,2} - V_{in,1} = V_{th,1} - V_{th,2} \\
 &= \frac{R_D}{2 \cdot R_{DS3}} \quad (\text{auch bei P-Mos})
 \end{aligned}$$

Gleichakt-Symmetrie $V_1 = V_{out,cm}$

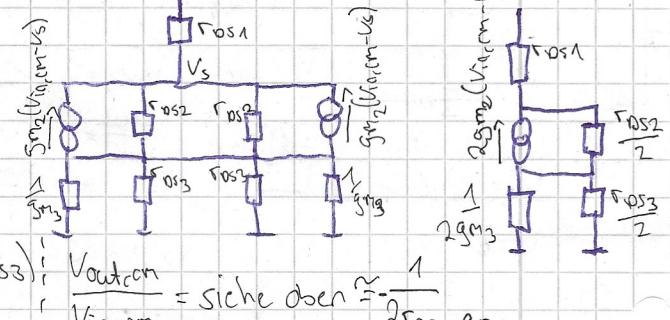

$$\frac{V_{out,cm}}{V_{i_0,cm}} = \text{siehe oben} \approx \frac{1}{2 \cdot R_{DS1} \cdot g_{m3}}$$

$$\begin{cases} V_{out} \leq V_{in} + V_{th} \\ V_{out} \geq V_{AS} - V_{th} \end{cases}$$

Verstärker

$$V_{out} = A(V_{in} + V_{ref})$$

Nicht Invertierender Verstärker

$$V_{out} = A[V_{in} - (V_{out} - V_{ref}) \frac{R_1}{R_1 + R_2}]$$

Invertierender Verstärker

$$V_{out} = -A(V_{in} + V_{ref})$$

Instrumentenverstärker

$$V_{out} = -\sum_{k=1}^3 V_{in,k} \frac{R_2}{R_1,k}$$

Summiervier

$$V_{out} = V_{in,1} \frac{R_2}{R_1} + V_{in,2} \frac{R_3}{R_1} + V_{in,3} \frac{R_3}{R_2}$$

Differenzverstärker

$$V_{out} = V_{in,p} \frac{R_1 + R_2}{R_1} - V_{in,n} \frac{R_2}{R_1}$$

Müller-Op

$$V_{out} = V_{ref} \cdot (1 + g_{m5} \cdot (r_{DS2} || r_{DS6}))$$

Müller Effekt

$$f_2 = \frac{g_{m5}}{2\pi C_L}$$

Komparator mit Hysterese

$$V_{out} = V_H \text{ if } V_{in} < V_L \text{ and } V_{out} = V_L \text{ if } V_{in} > V_H$$

Bandpass

$$V_{out} = H(j\omega) \cdot V_{in}$$

Hochpass

$$V_{out} = H(j\omega) \cdot V_{in}$$

Tiefpass

$$V_{out} = H(j\omega) \cdot V_{in}$$

Eingangsverstärkung:

$$A = -g_{m2} (r_{DS2} || r_{DS6})$$

Bandpass:

$$H(j\omega) = \frac{R_2 - j\omega R_1 C_1}{R_1 + j\omega R_1 C_1 + j\omega R_2 C_2} = A_0 \frac{R_2}{R_1}$$

Allgemeiner Verstärker:

$$A \rightarrow \infty: V_{out} = A \cdot V_{in}$$

$$A \text{ endlich: } V_{out} = A (V_{in+} - V_{in-})$$

$$\text{Offset: } V_{out} = V_{out,los} + V_{out,V_{in}=0}$$

Invertierender Verstärker mit Offset:

$$A \rightarrow \infty: V_{out} = -\frac{R_2}{R_1} V_{in+} (1 + \frac{R_2}{R_1}) V_{os}$$

$$A \text{ endlich: } V_{out} = -\frac{(R_2)}{1 + \frac{1}{A} (1 + \frac{R_2}{R_1})} V_{in+} (1 + \frac{R_2}{R_1}) \frac{V_{os}}{1 + \frac{1}{A} (1 + \frac{R_2}{R_1})}$$

Rail-to-Rail: $V_{out,\max} \approx \text{Versorgungsspannung}$

Müller Op: Wenn als Spannungsfolger:

$$V_{in} \leq V_{DD} - V_{AS1} - V_{AS2} + V_{IN}$$

$$V_{in} \geq V_{AS3} - V_{TH}$$

$$R_L > \frac{V_{out}}{V_{DD}}$$

$$V_{out} = V_{out}$$

$$V_{out} \geq V_{DD} - V_{AS3} + V_{TH}$$

$$V_{out} \leq V_{DD} - V_{AS1} + V_{TH}$$

Stabilität:

$$A = \frac{V_{out}}{V_{in}} = \frac{R_2}{R_1} \frac{1}{1 + (\omega R_1 C)^2} (1 - \frac{j}{\omega R_1 C})$$

$$|H(j\omega)| = \frac{R_2}{R_1} \frac{1}{1 + (\frac{1}{\omega R_1 C})^2}$$

$$\varphi(H(j\omega)) = -180^\circ + \arctan(\frac{1}{\omega R_1 C})$$

$$\varphi(H(j\omega)) = -180^\circ + \arctan(-\omega R_1 C)$$

$$f_g = \frac{1}{2\pi R_1 C}$$

Stabilität:

$$A = \frac{V_{out}}{V_{in}} = \frac{R_2}{R_1} \frac{1}{1 + (\omega C R)^2} (1 - j\omega C R)$$

$$|H(j\omega)| = \frac{R_2}{R_1} \frac{1}{1 + (\omega C R)^2}$$

$$\varphi(H(j\omega)) = -180^\circ + \arctan(-\omega C R)$$

$$f_g = \frac{1}{2\pi C R}$$